

LIC →

- Q ADC, DAC - Types (working explain)
- Q Functional block diag of 555 timer IC
- Q Monostable multivibrator & Astable (also) with waveform & IC pin configuration
- Q Design of lowpass filter (1<sup>st</sup> & 2<sup>nd</sup> order)
- Q Sine wave oscillator (Wien bridge) - working & eq  $\frac{1}{2\pi\sqrt{6RC}}$
- Q Functional block diag of series voltage regulator
- Q Design voltage regulator using 7805 - for current source.